



ELA 1110

**DIODE**

# Introduction

- The semiconductor diode is created by simply joining an n -type and a p -type material together.
- At the instant the two materials are “joined” the electrons and the holes in the region of the junction will combine, resulting in a lack of free carriers in the region near the junction, as shown in Fig.1.
- Diode Symbol with the defined polarity and the current direction and the current direction is shown in fig.2.

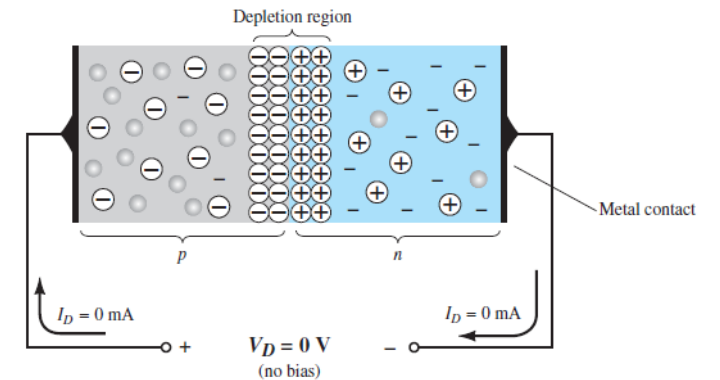


Fig. 1: p–n junction with no external bias

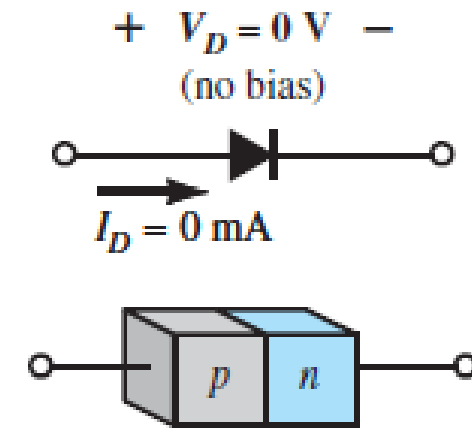


Fig. 2: Diode Symbol

# Operation

- In the absence of an applied bias across a semiconductor diode, the net flow of charge in one direction is zero.
- Under reverse bias, external potential is applied across the p – n junction such that the positive terminal is connected to the n -type material and the negative terminal is connected to the p -type material as shown in fig.4.
- The current that exists under reverse-bias conditions is called the reverse saturation current and is represented by  $I_S$ .
- Depletion region widens in reverse bias operation.
- A forward-bias or “on” condition is established by applying the positive potential to the p -type material and the negative potential to the n -type material as shown in Fig.3.
- The application of a forward-bias potential reduces the width of the depletion region.

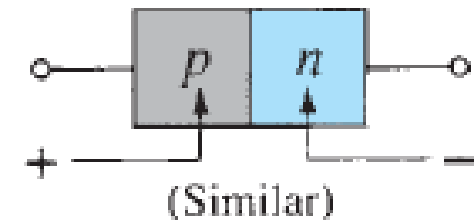
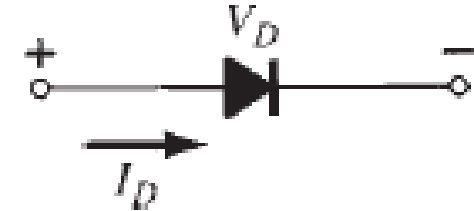


Fig. 3: Forward-biased p-n junction

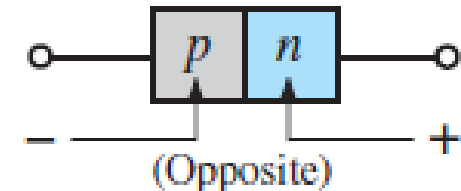
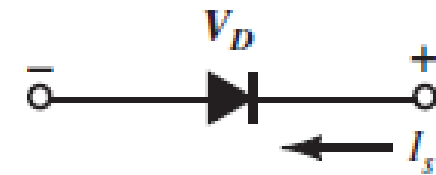


Fig.4: Reverse-biased p-n junction

# Diode Equation

- The general characteristics of a semiconductor diode can be defined by the following equation, referred to as Shockley's equation, for the forward- and reverse-bias regions.

$$I_D = I_s(e^{V_D/nV_T} - 1)$$

Where,

$I_s$  is the reverse saturation current

$V_D$  is the applied forward-bias voltage across the diode

$\eta$  is an ideality factor, ( Value:1to2)

$V_T$  is called the thermal voltage

- The thermal Voltage is given as

$$V_T = \frac{kT_K}{q}$$

Where,

$k$  is Boltzmann's constant  $1.38 \times 10^{-23}$  J/K

$T_K$  is the absolute temperature in kelvins =  $273 +$  the temperature in  $^{\circ}\text{C}$

$q$  is the magnitude of electronic charge  $1.6 \times 10^{-19}$  C


Example1: At a temperature of 27°C, determine the thermal voltage  $V_T$ .

Solution:

$$\begin{aligned} T &= 273 + ^\circ\text{C} = 273 + 27 = 300 \text{ K} \\ V_T &= \frac{kT_K}{q} = \frac{(1.38 \times 10^{-23} \text{ J/K})(300 \text{ K})}{1.6 \times 10^{-19} \text{ C}} \\ &= 25.875 \text{ mV} \cong 26 \text{ mV} \end{aligned}$$
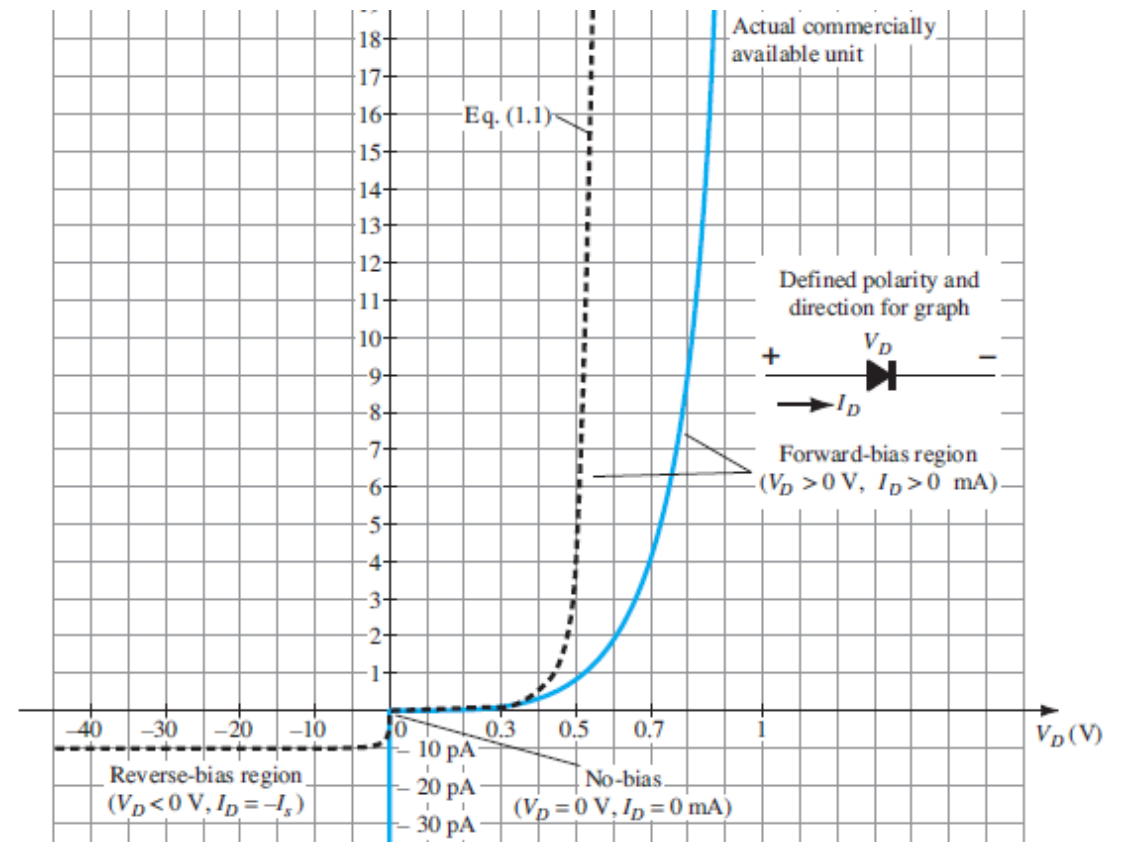
# V-I Characteristics of Diode

- For negative values of  $V_D$ ,
  - $I_D = -I_S$
- At  $V_D = 0V$ ,
  - $I_D = I_S(e^0 - 1) = I_S(1 - 1) = 0 \text{ mA}$
- The defined direction of conventional current for the positive voltage region matches the arrowhead in the diode symbol.
- The actual reverse saturation current of a commercially available diode will normally be measurably larger than that appearing as the reverse saturation current in Shockley's equation.



# Breakdown Region

- In V-I characteristics of diode, there is a point where the application of too negative a voltage with the reverse polarity will result in a sharp change in the characteristics, as shown in Fig. 5
- The reverse-bias potential that results in this dramatic change in characteristics is called the breakdown potential and is given the label  $V_{BV}$
- The current increases at a very rapid rate in a direction opposite to that of the positive voltage region.
- The two break-down mechanism in diode are:
  - Avalanche Breakdown
  - Zener Breakdown

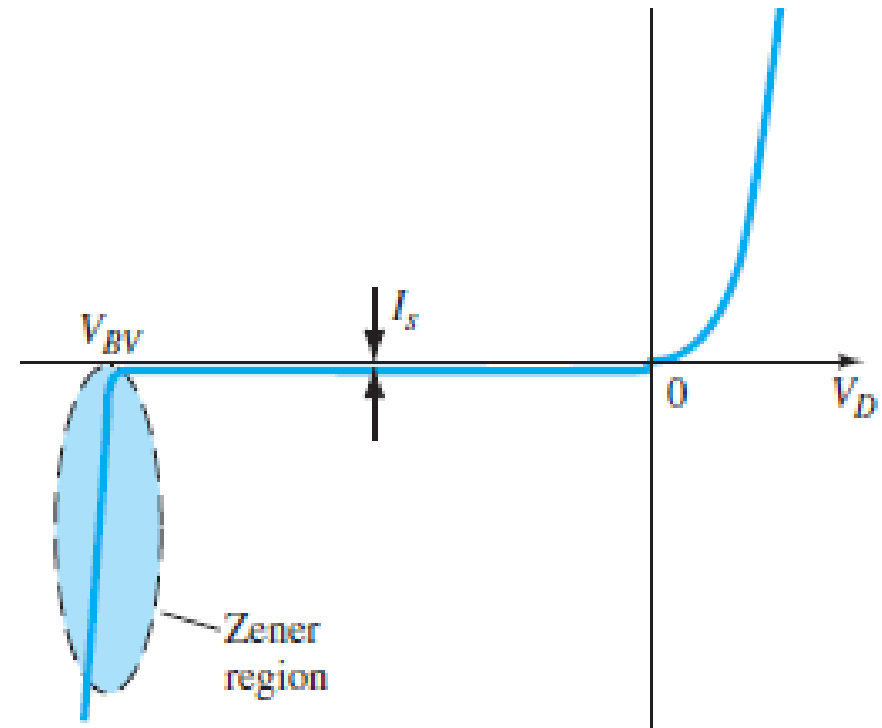


Fig. 5: Breakdown region.

# Diode Resistance

- As the operating point of a diode moves from one region to another the resistance of the diode will also change due to the nonlinear shape of the characteristic curve.
- **DC or Static Resistance**
  - The application of a dc voltage to a circuit containing a semiconductor diode will result in an operating point on the characteristic curve that will not change with time.
  - The resistance of the diode at the operating point can be found by the following equation.

$$R_D = \frac{V_D}{I_D}$$




- **AC or Dynamic Resistance**

- The dc resistance of a diode is independent of the shape of the characteristic in the region surrounding the point of interest.
- A straight-line drawn tangent to the curve through the  $Q$ -point as shown in Fig. 6.
- It will define a particular change in voltage and current that can be used to determine the *ac* or dynamic resistance for this region of the diode characteristics

$$r_d = \frac{\Delta V_d}{\Delta I_d}$$

Where,  $\Delta$  signifies a finite change in the quantity.

- The lower the  $Q$ -point of operation (smaller current or lower voltage), the higher is the ac resistance.

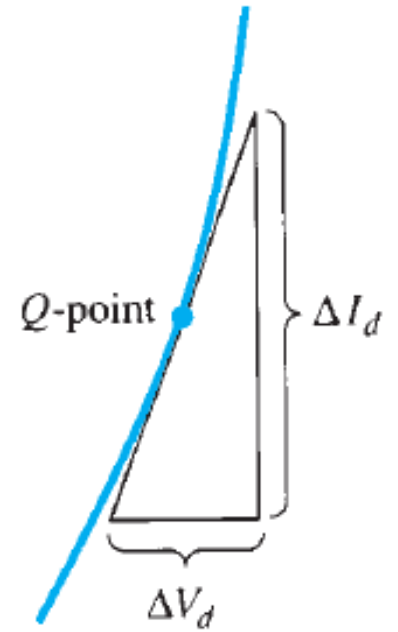

**Fig.6: Determining the ac resistance at a  $Q$ -point.**

# Diode Models

- An equivalent circuit/model is a combination of elements properly chosen to best represent the actual terminal characteristics of a device or system in a particular operating region.
- Once the equivalent circuit is defined, the device symbol can be removed from a schematic and the equivalent circuit inserted in its place.
- The various models used to represent diode are:
  - Piece Wise Equivalent Circuit
  - Simplified Equivalent Circuit
  - Ideal Equivalent Circuit

# Piece Wise Linear Model

- In this technique , the ideal diode is included to establish that there is only one direction of conduction through the device.
- A reverse-bias condition will result in the open-circuit state for the device.
- It can be obvious from Fig.7 that the straight-line segments do not result in an exact duplication of the actual characteristics especially in the knee region.

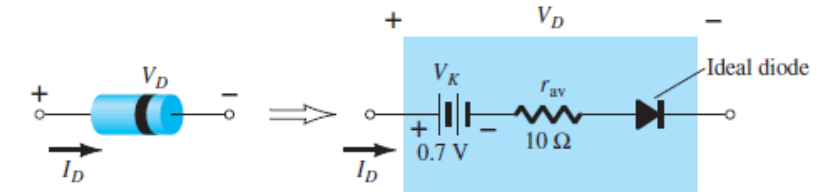


Fig.7: Components of the piecewise-linear equivalent circuit.

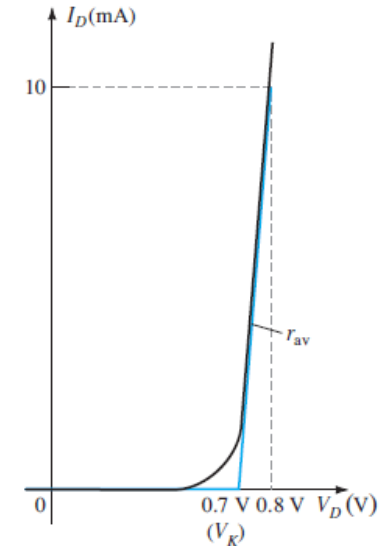


Fig. 8: Defining the piecewise-linear equivalent circuit using straight-line segments

# Simplified Equivalent Circuit

- For most applications, the resistance  $r_{av}$  is sufficiently small to be ignored in comparison to the other elements of the network.
- The reduced equivalent circuit appears in the shown in fig.9.
- It states that a forward biased silicon diode in an electronic system under dc conditions has a drop of 0.7V.

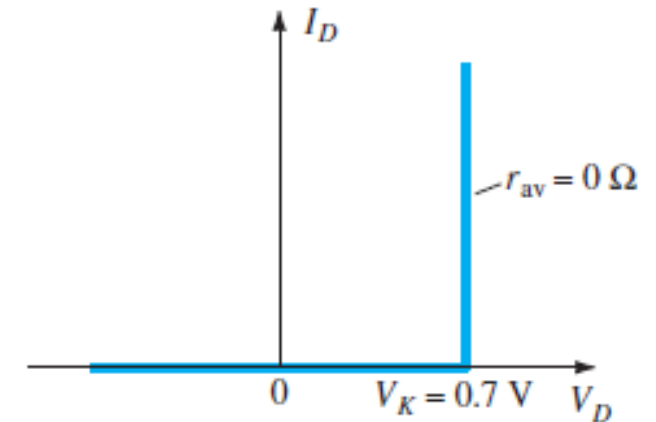
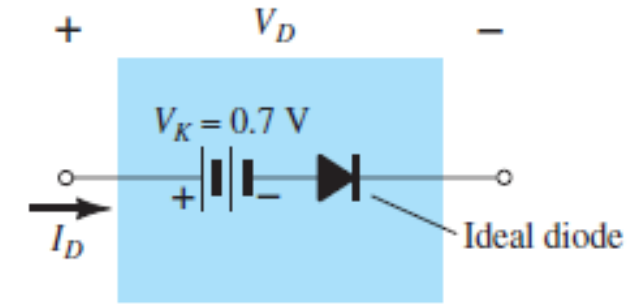


Fig.9: Simplified equivalent circuit for the silicon semiconductor diode.

# Ideal Equivalent Circuit

- In this case the equivalent circuit will be reduced to that of an ideal diode as shown in Fig. 10 with its characteristics.

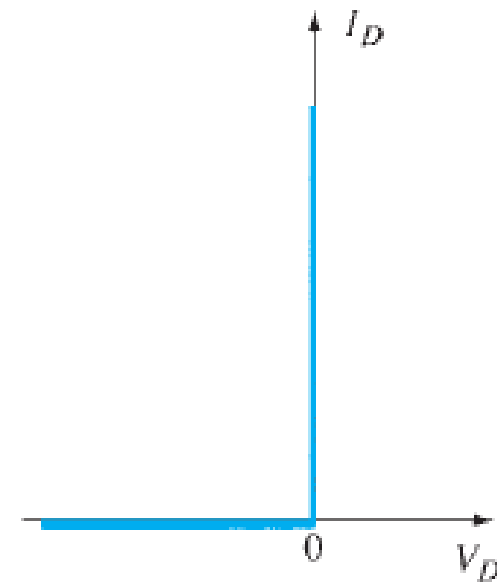
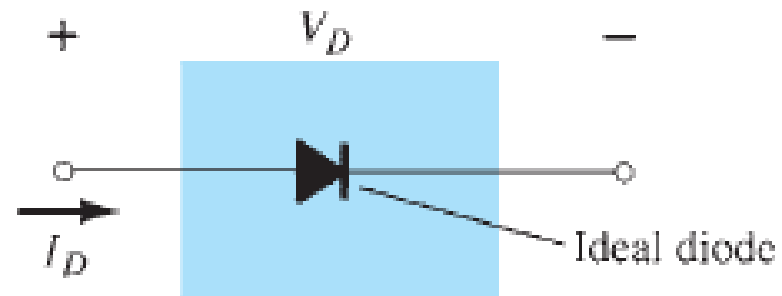
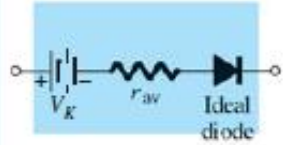
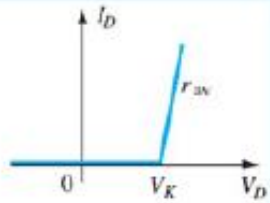
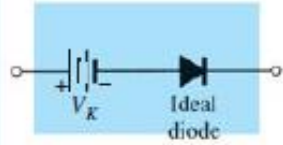
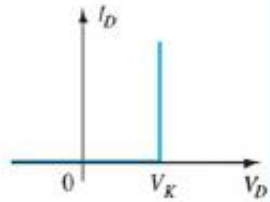

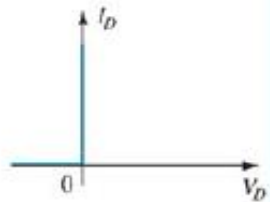


Fig.10: Ideal diode and its characteristics.

- Table 1 : Diode Equivalent Circuits (Models)

| Type                   | Conditions   | Model  | Characteristics  |
|------------------------|--|--|--|
| Piecewise-linear model |  |   |   |
| Simplified model       | $R_{\text{network}} \gg r_{\text{av}}$                                 |   |   |
| Ideal device           | $R_{\text{network}} \gg r_{\text{av}}$<br>$E_{\text{network}} \gg V_K$ |  |  |

# Example

Q. For the series diode configuration of Fig. 11 , determine  $V_D$  ,  $V_R$  , and  $I_D$  using the following models: (Given  $r_{AV} = 10\Omega$ )

- (a) Piece wise linear Model
- (b) Constant Voltage drop Model
- (c) Ideal Diode Model

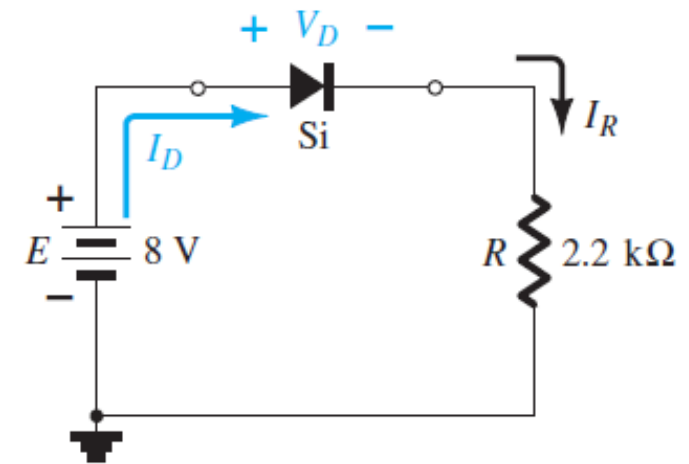



Fig.11

Solution :- (a) Using Piecewise linear model

$$I_D = I_R = I$$

$$V_D = 0.7$$

$$r_{av} = 10\Omega \text{ (Given)}$$

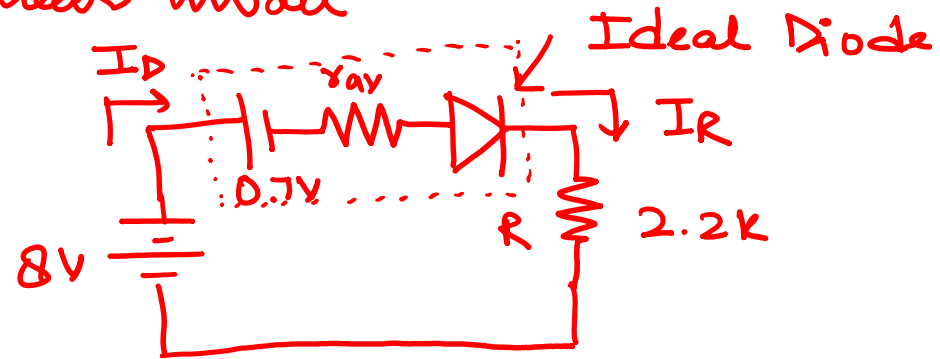

$$8 - 0.7 - I r_{av} - I(2.2k) = 0$$

$$7.3 - I(10 + 2200) = 0$$

$$I = \frac{7.3}{2210} = 0.00330 = 3.30\text{mA}$$

$$I_D = 3.30\text{mA}$$

$$V_R = I \times R = 3.30 \times 2.2 = 7.26\text{V}$$

$$V_R = 7.26\text{V}$$



⑥ Using Simplified Equivalent Circuit / Constant Voltage

$$V_D = 0.7V$$

$$I_D = I_R = I$$


$$8 - 0.7 - IR = 0$$

$$I = \frac{7.3}{2.2} = 3.32mA$$

$$I_D = 3.32mA$$

$$V_R = I.R = 3.32 \times 2.2 = 7.30V$$

$$V_R = 7.30V$$

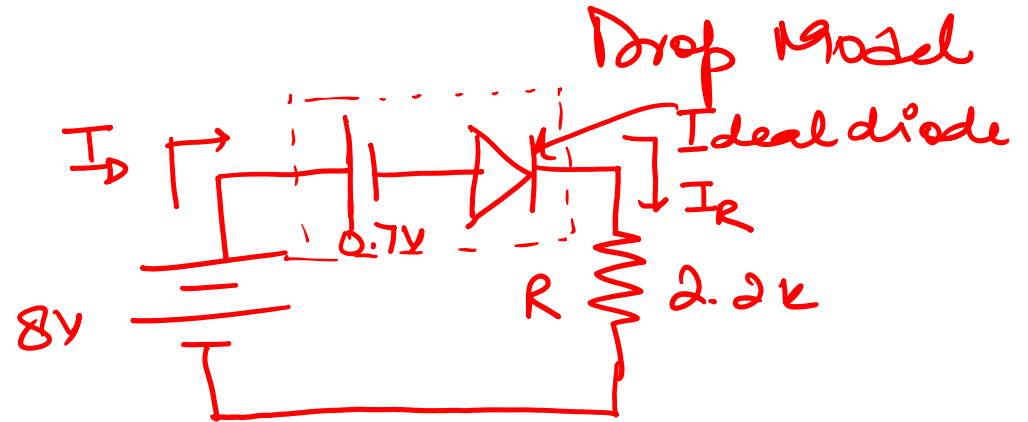

c) Using Ideal Diode Model

$$V_D = 0$$

$$I_D = I_R = I$$


$$8 - I \cdot (2.2) = 0$$

$$I = \frac{8}{2.2} = 3.64 \text{ mA}$$

$$I_D = 3.64 \text{ mA}$$

$$V_R = I \cdot R = 3.64 \times 2.2 = 8 \text{ V}$$

$$V_R = 8 \text{ V}$$

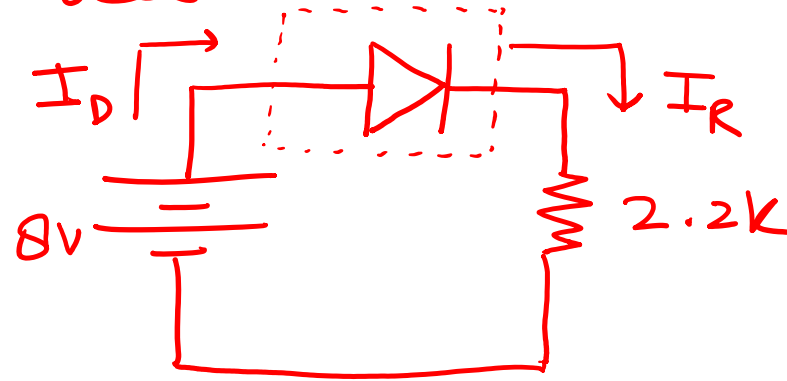

# Problems

Q.1 Determine the thermal voltage for a diode at a temperature of 20. Also, find the diode current if  $I_S = 40 \text{ nA}$ ,  $n = 2$  and the applied bias voltage is 0.5 V.

Q.2 Given a diode current of 8 mA and  $n = 1$ , find  $I_S$  if the applied voltage is 0.5 V and the temperature is room temperature ( $25^\circ\text{C}$ ).

Q.3 Given a diode current of 6 mA,  $V_T = 26 \text{ mV}$ ,  $n = 1$ , and  $I_S = 1 \text{ nA}$ , find the applied voltage  $V_D$ .

Q.4 Determine the static or dc resistance of the commercially available diode of Fig. 1.15 at a forward current of 4 mA.