



# Operational Amplifier

---

UNIT-III

# Introduction

---

- Operational amplifier (op-amp)
  - Very high gain differential amplifier
  - High input impedance
  - Low output impedance
- Applications
  - Oscillators
  - Filters
  - Instrumentation Amplifier
  - A to D Converters
  - Zero Crossing Detectors
  - Precision Rectifiers

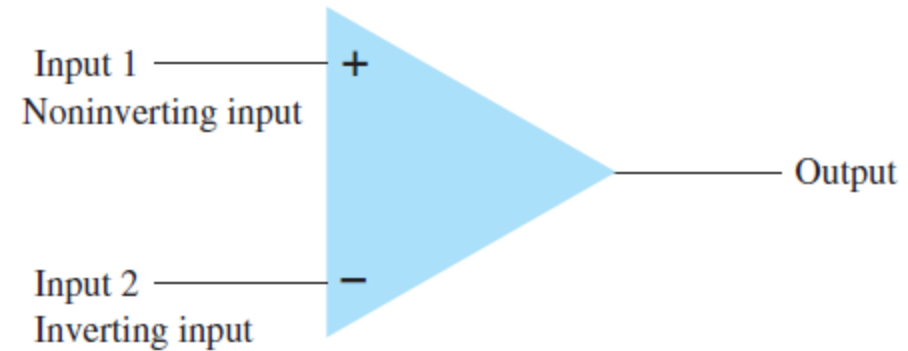


Fig.1: Single- Ended Operation

# Single Ended Input

---

- Single-ended input operation results when the input signal is connected to one input with the other input connected to ground.

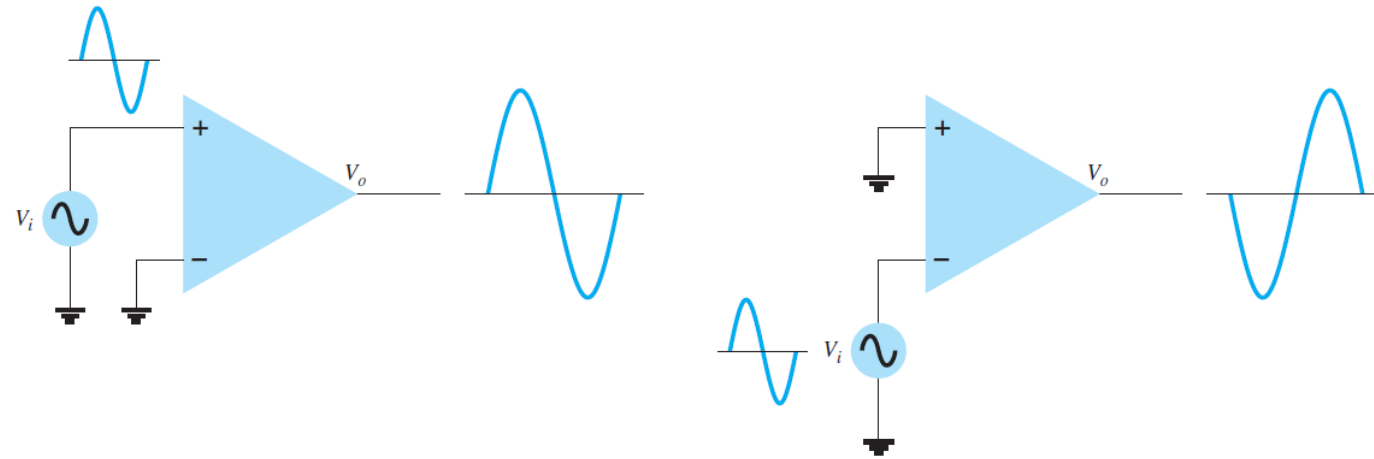


Fig.2: Single- Ended Operation

# Double-Ended (Differential) Input

---

- In addition to using only one input, it is possible to apply signals at each input.
- Resulting configuration is called double-ended operation.

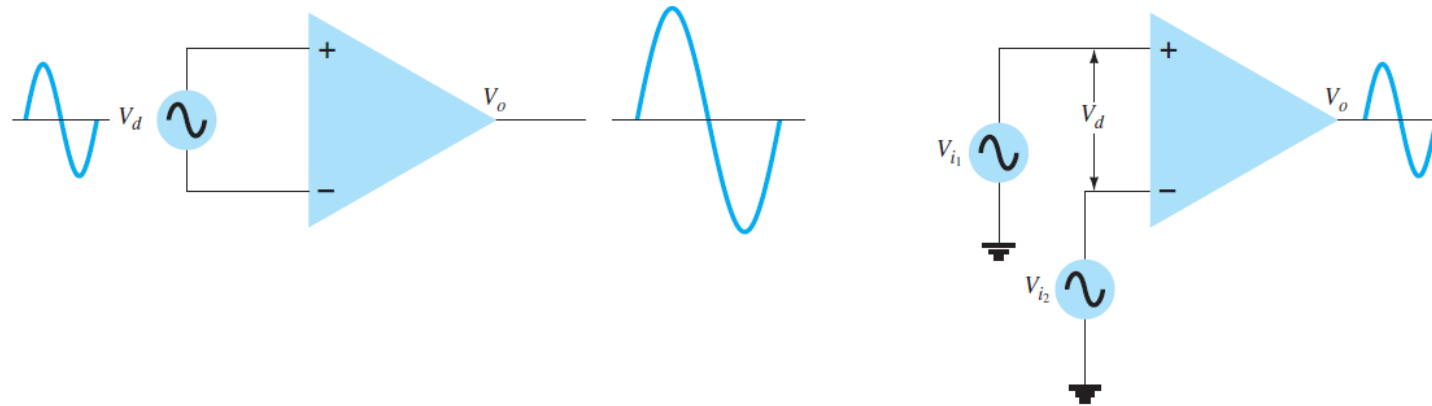


Fig.3: Double- Ended Operation

# Op-Amp Basics

---

- An operational amplifier having
  - Very high gain
  - Very high input impedance (typically a few megohms)
  - Low output impedance (less than 100 )
  - High CMRR (Common mode rejection ratio)
- Fig.4 shows a basic op-amp unit.
- Input terminals:
  - Inverting Input (marked with “-” )
  - Non-Inverting Input ( marked with “+”)

$$V_O = A(V^+ - V^-)$$

A : open loop gain of op-amp



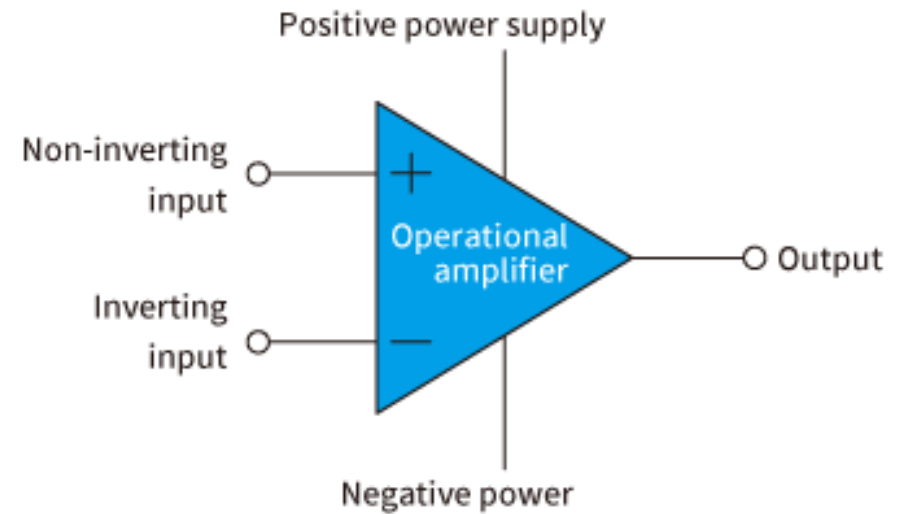


Fig.4: *Basic op- amp*

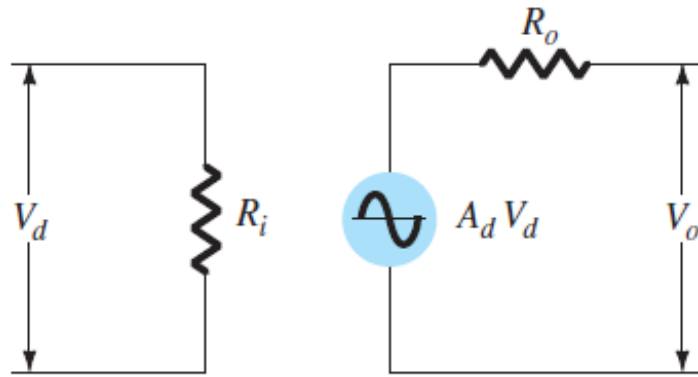

(a) Practical

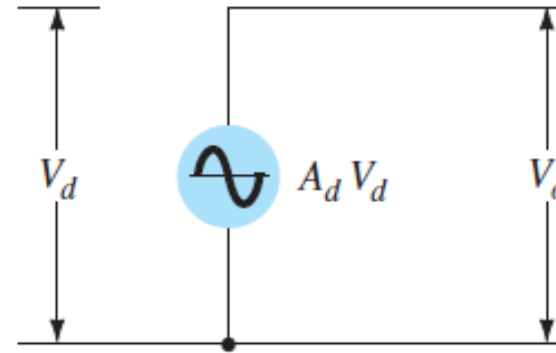

(b) Ideal

Fig.5: AC equivalent of op- amp circuit

# Op-Amp Characteristics

---

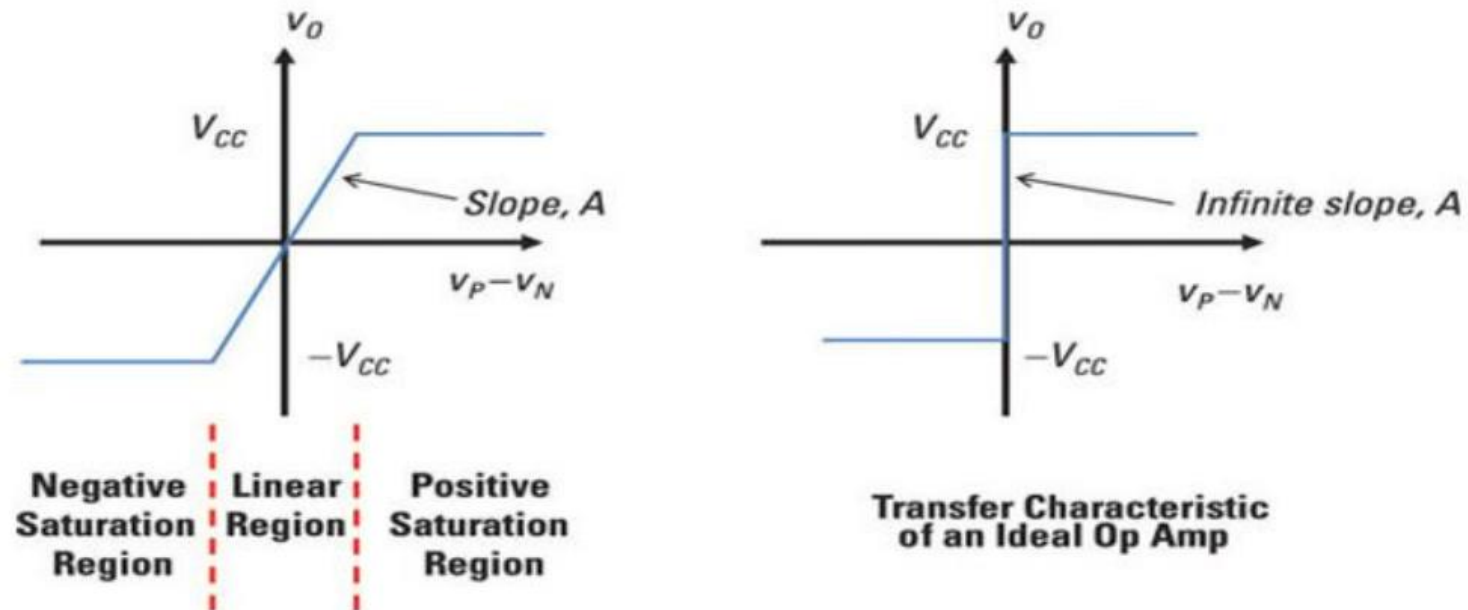


Fig.6: Ideal vs. practical characteristics of Op-amp

---

Parameter	Ideal	General Purpose 741 Op-Amp
Voltage Gain, $G$	$\infty$	$1 \times 10^5$
Output Impedance, $R_o$	0	$75 \Omega$
Input Resistance, $R_{in}$	$\infty$	$2 \text{ M}\Omega$
Offset Current, $I_{io}$	0	$20 \text{ nA}$
Offset Voltage, $V_{io}$	0	$2 \text{ mV}$
Bandwidth, BW	$\infty$	$1 \text{ MHz}$
Slew Rate, SR	$\infty$	$.7 \text{ V/uS}$



# Working Principle

---

## OPEN LOOP OPERATION

- The ideal op-amp amplifies the difference between the two applied input (i.e. at inverting and non inverting) signals.
- This difference between the two input signal is called the differential input voltage.
- The output voltage of open loop op-amp is given as

$$V_{out} = A_{OL}(V^+ - V^-)$$

Where,  $A_{OL}$  is open loop of op-amp

- In open loop, op-amp works as comparator

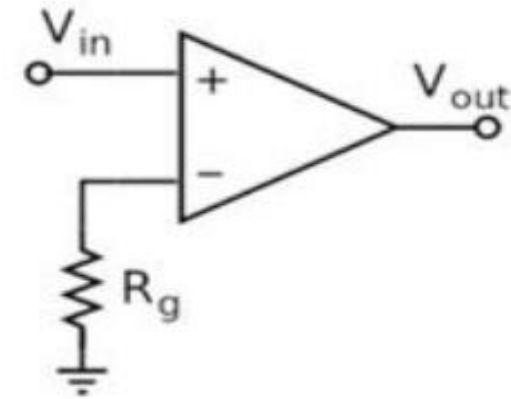


Fig.7: Open-loop operation

---

## CLOSED LOOP OPERATION

- Feedback is introduced in the closed-loop configuration.
- This feedback path feeds the output signal back to input side.
- The output voltage of closed loop op-amp is given as

$$V_{out} = A_{CL}(V^+ - V^-)$$

Where,  $A_{CL}$  is the closed-loop gain

- Feedback circuit connected to op-amp determines  $A_{CL}$
- Types of feedback
  - Positive (used in Oscillators)
  - Negative (used in Amplifiers)

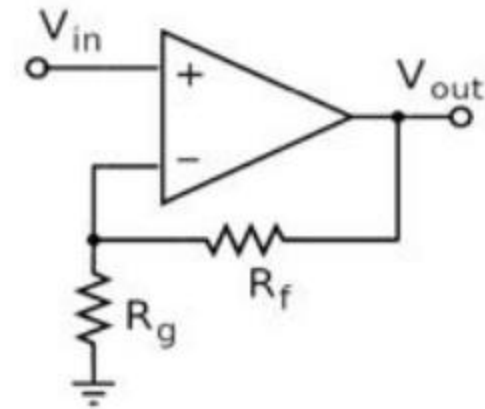


Fig.8: Closed-loop operation

# Concept of Virtual Short

---

- Basically the “short” between two points that are imaginary.
- In context to op-amp, virtual short means, the voltage at inverting terminal tracks the voltage at non-inverting terminal under negative feedback ( $V_+ = V_-$ )
- As we know that,  $\text{Gain} = \frac{V_{out}}{V_{in}}$
- As ideal gain is infinite, hence  $V_{in} = 0$

$$V_{in} = V_+ - V_-$$

$$V_+ = V_-$$

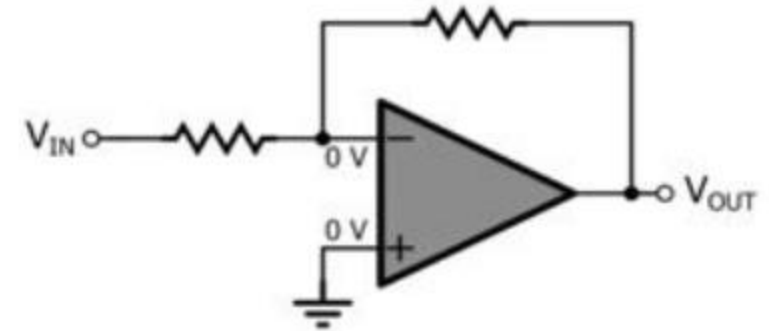


Fig.9: Virtual Ground in negative feedback

# Electrical Parameters of Op-amp

---

**Input bias current:** Average current flows in inverting & no-inverting terminal.

**Input & output impedance:** Resistance offered by input and output terminals to varying voltages.

**Open loop gain:** Overall voltage gain of amplifier.

**Input offset voltage:** It is the voltage that must be applied between the two terminals of op-amp to make then output zero.

**Input offset current:** The algebraic difference between the current in to the inverting and non-inverting terminal.

# Op-Amp IC

---

- The most commonly used op-amp is IC741.
- It is a 8-pin dual-in-line package with a pinout shown above.
  - Pin 1: Offset null
  - Pin 2: Inverting input terminal
  - Pin 3: Non-inverting input terminal
  - Pin 4:  $-V_{CC}$  (negative voltage supply)
  - Pin 5: Offset null
  - Pin 6: Output voltage
  - Pin 7:  $+V_{CC}$  (positive voltage supply)
  - Pin 8: No Connection

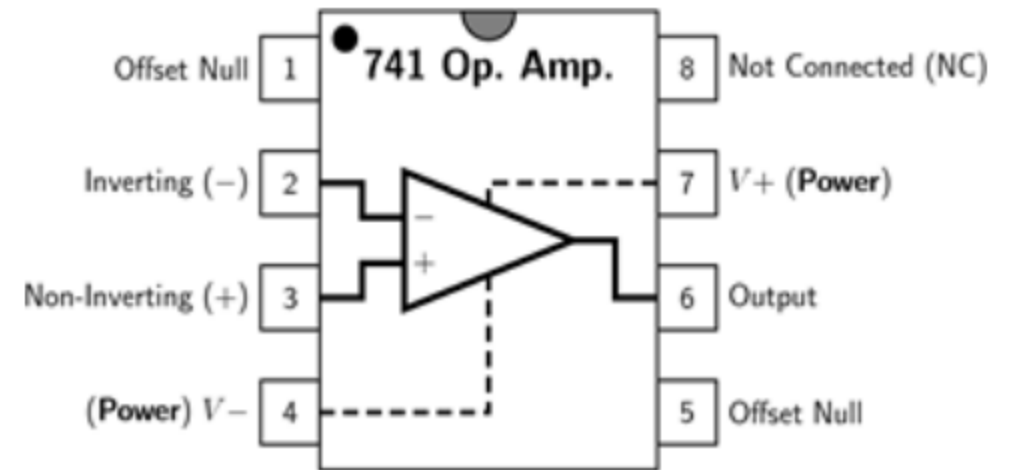


Fig.10: Pin Diagram of LM741

# Applications

---

- Operational amplifiers are popular building block, finds application in most of the consumer and industrial electronic system.
- They can be configured as
  - Inverting Amplifier
  - Non-Inverting Amplifier
  - Buffer (Voltage follower)
  - Summing Amplifier
  - Difference Amplifier
  - Differentiator
  - Integrator
  - Filters
  - Comparator etc.

# Inverting Amplifier

---

$$V_o = -\frac{R_f}{R_1} V_1$$

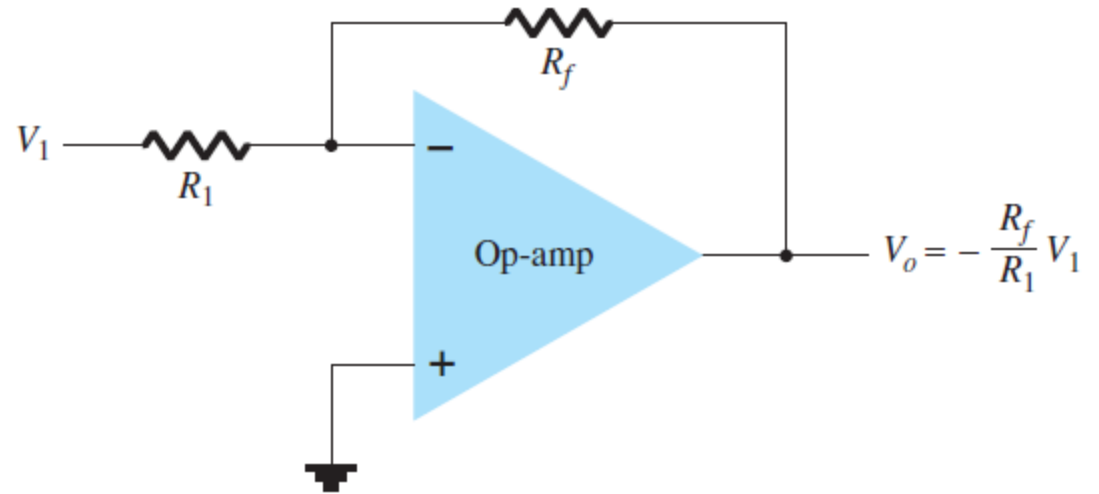


Fig.11: Inverting Amplifier

# Non Inverting Amplifier

---

$$\frac{V_o}{V_1} = \frac{R_1 + R_f}{R_1} = 1 + \frac{R_f}{R_1}$$

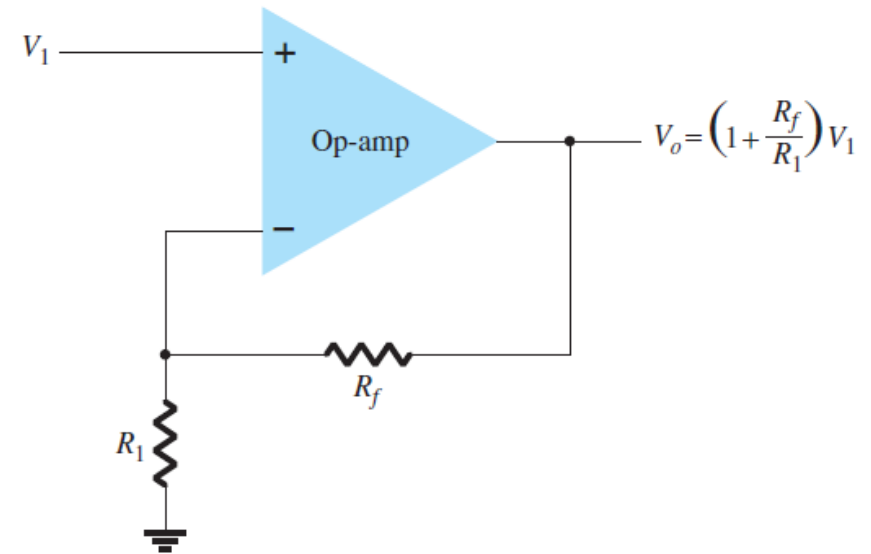


Fig.12: Non-Inverting Amplifier



# Unity Follower

---

It provides a gain of unity (1) with no polarity or phase reversal.

$$V_o = V_i$$

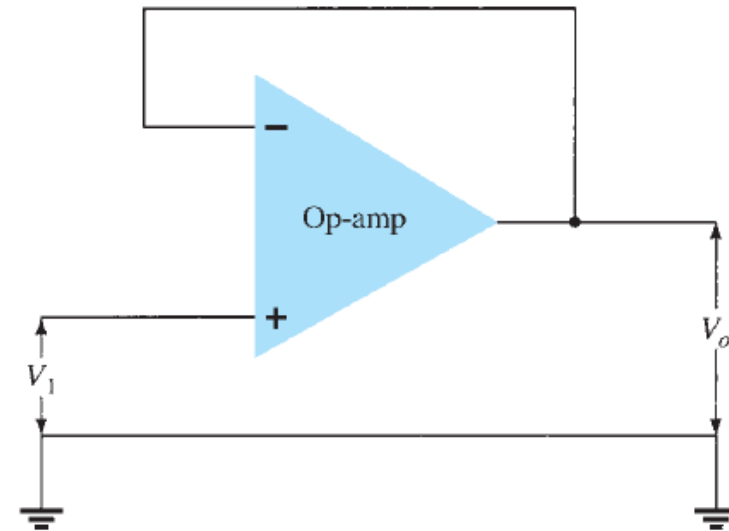


Fig.13: Unity Follower

# Summing Amplifier

---

$$V_o = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3\right)$$

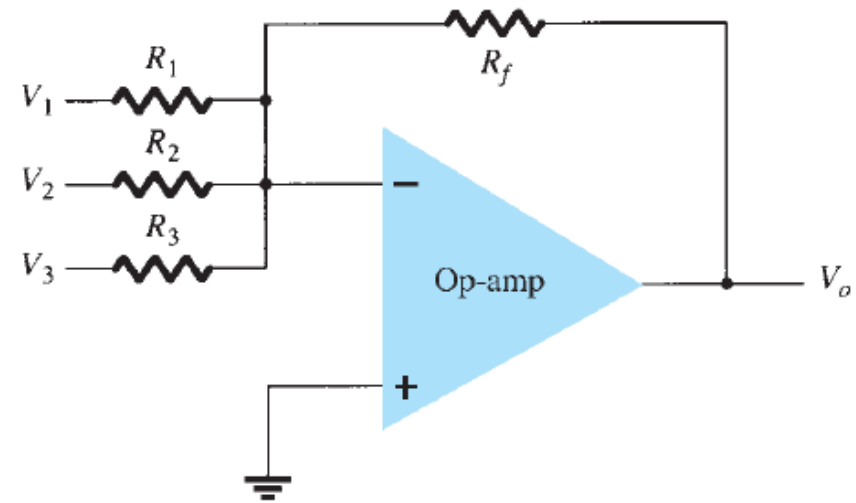


Fig.14: Summing Amplifier

# Difference Amplifier

---

If  $R_1 = R_2$  and  $R_f = R_g$ :

$$V_{\text{out}} = \frac{R_f}{R_1} (V_2 - V_1)$$

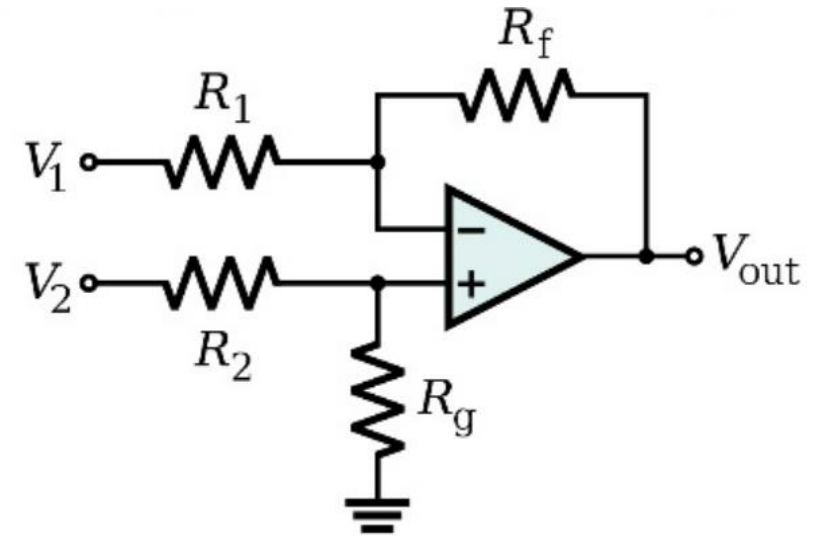


Fig.15: Difference Amplifier

# Integrator

---

$$v_o(t) = -\frac{1}{RC} \int v_1(t) dt$$

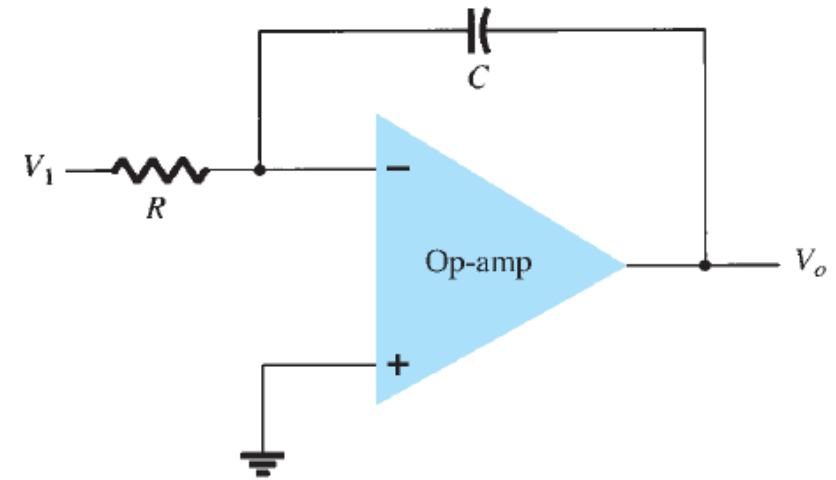


Fig.16: Integrator

# Differentiator

---

$$v_o(t) = -RC \frac{dv_1(t)}{dt}$$

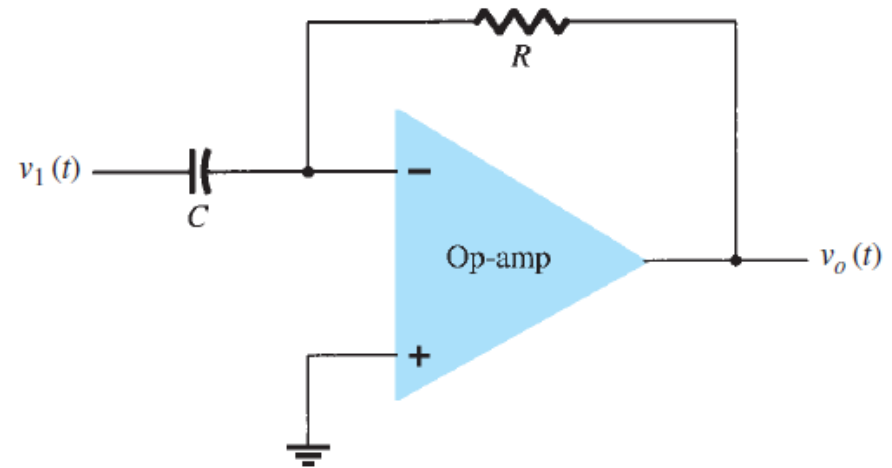


Fig.17: Differentiator